

RIGA TECHNICAL UNIVERSITY
FACULTY OF POWER AND ELECTRICAL ENGINEERING
INSTITUTE OF INDUSTRIAL ELECTRONICS
AND ELECTRICAL ENGINEERING

IVARS RANKIS
JANIS ZAKIS
ANASTASIA ZHIRAVETSKA

POWER ELECTRONICS

RTU Press
Riga 2018

Contents

Preface	5
Introduction	6
1. Elements of semiconductor converters and the basic conceptions	11
1.1. Fundamental electrical parameters.....	11
1.2. Properties of the passive reactive elements	15
1.3. Properties of diode and its characteristics	20
1.4. Bipolar transistor (BT) as an element of powerful converter.....	29
1.5. Thyristors.....	35
1.6. Power MOSFETs.....	47
1.7. Insulated Gate Bipolar Transistors IGBT	49
1.8. Thermal mode calculations of semiconductor elements.....	52
1.9. Control and protection of transistors	55
Review questions	58
Tasks.....	61
2. Line-frequency converters (LFC).....	65
2.1. Diode rectifiers.....	65
2.1.1. Rectifier circuits	65
2.1.2. Single-phase bridge rectifier.....	67
2.1.3. Single-phase centre-tap rectifier with transformer	72
2.1.4. Three-phase half-cycle (centre-tap) rectifier.....	74
2.1.5. Three-phase full-bridge rectifier.....	78
2.1.6. Six-phase rectifier.....	80
2.1.7. Twelve-pulse rectifier	83
2.1.8. Ripple factor of the rectified voltage.....	86
2.1.9. Form of the network current.....	88
2.1.10. The process of current commutation	90
Review questions	96
Tasks.....	99
2.2. Line-frequency phase controlled converters	101
2.2.1. Control characteristics.....	101
2.2.2. Inverting operation mode of the controlled rectifiers.....	105
2.2.3. Commutation processes in the controlled rectifiers	108
2.2.4. Power factor of the controlled rectifier.....	114
2.2.5. Reversible rectifiers.....	120
2.3. Cycloconverters	125
2.4. AC voltage controllers.....	133
2.5. Control principles of the line-frequency converters	140
Review questions	144
Tasks.....	146
3. Switch-mode dc-dc converters	149
3.1. DC/DC converters.....	149
3.1.1. Step-down (buck) converter.....	149
3.1.2. Step-up (boost) converter.....	152

3.1.3. Improvement of the converter characteristics with autotransformer	154
3.1.4. Buck-boost converter	155
3.1.4.1. Conventional topology	155
3.1.4.2. Cuk converter	157
3.1.4.3. Buck-boost converter of the load voltage of the same polarity	158
3.1.4.4. Buck-boost converter of commutated configuration.....	159
3.1.5. Input and output filters	159
3.1.6. Multi-phase buck converters	165
3.1.7. Discontinuous load current operation mode of buck converter	168
3.1.8. Full-bridge DC-DC converter	172
3.1.9. Implementation of qZ Source network.....	177
3.1.10. DC-DC converters with thyristors	180
3.1.11. Operation of transistor switch in real circuit	183
3.1.11.1. Process of transistor switching	183
3.1.11.2. Safe operation area (SOA)	187
3.1.11.3. Improvement of the turn-off process	189
3.1.11.4. Improvement of the turn-on process	194
3.1.12. Isolated DC-DC power supply	196
3.1.13. Calculation of the DC smoothing inductor.....	201
Review questions	205
Tasks.....	208
3.2. Voltage and current source inverters (VSI and CSI)	212
3.2.1. Single-phase voltage source inverters (VSI)	212
3.2.2. Features of bridge-type single-phase voltage source inverter.....	214
3.2.3. Features of neutral point transformer based single-phase inverter.....	218
3.2.4. Single-phase voltage source inverter control.....	220
3.2.5. PWM-regulated single-phase full-bridge voltage source inverter	225
3.2.6. Three-phase voltage source inverter operation principle	229
3.2.7. Three-phase voltage source inverter control.....	234
3.2.8. Multi-level voltage source inverters.....	240
3.3. Current source inverters.....	242
3.3.1. Operation principle of current source inverter	242
3.3.2. Three-phase current source inverters	248
3.3.3. Control of the voltage of current source inverter	252
3.4. Resonance inverters	253
3.5. Commutated converter control systems.....	257
Review questions	262
Tasks.....	265
4. Network power converters with free commutation capacities	267
4.1. Rectifier — power conditioner.....	267
4.2. Rectifier — network current waveform corrector	279
Review questions	285
Tasks.....	287
References.....	288